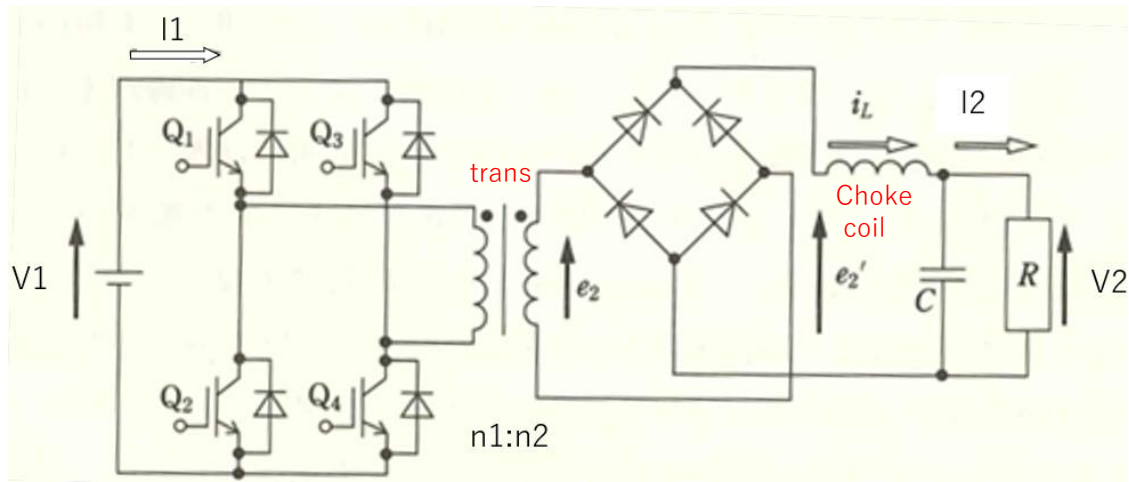




$$e_2 = \frac{n_2}{n_1} V_1$$

$$V_2 = \frac{T_{on}}{T_{on} + T_{off}} e_2 = \frac{n_2}{n_1} \frac{T_{on}}{T_{on} + T_{off}} V_1$$


$$V_1 = L_t \frac{di_m}{dt}$$

$$\frac{di_2}{dt} = \frac{e_2 - V_2}{L_c} \quad \frac{di_L}{dt} = \frac{e_2}{L_c}$$

$$i_2' = \frac{n_2}{n_1} i_2$$

L_t : Self-inductance of the transformer viewed from the V_1 side

L_c : Self-Inductance of choke-coil

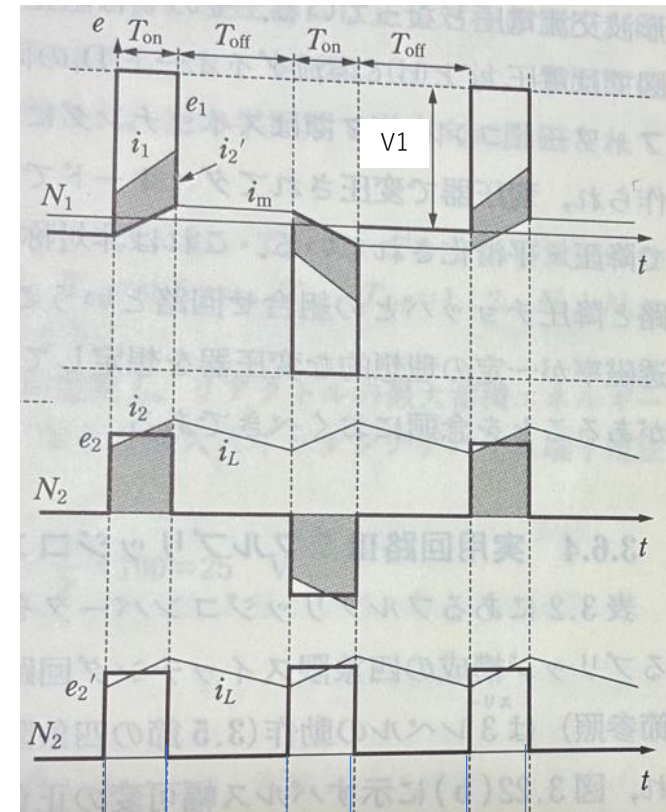

Q1	on	off	off	on	on	off
Q2	off	on	on	off	off	on
Q3	off	off	on	on	off	off
Q4	on	on	off	off	on	on